

## Chapter 20

### Electric Circuits

## Electromotive Force

- emf
- Maximum potential difference provided by a power source

## Current


- Rate at which electrical charges move through a given area
- Units => C/s = Ampere (A)

## Example

- If the current through a light is 230 mA, how much charge passes a specific point in 12 seconds?
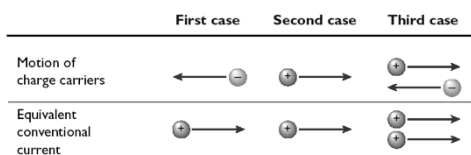
## Conventional Current

- Charge carriers are presumed to be positive



## Types of current

- Direct Current
  - Charges move in only one direction
- Alternating Current
  - Motion of charges changes continuously from forward to reverse

## Resistance

- **The opposition to the flow of current in a conductor**
- **Units => V/A = Ohms ( $\Omega$ )**

## Ohm's Law

- **Resistance is constant over a wide range of potential differences**
  - Most metals
  - Does not include all materials
    - diodes

## Resistors

- **Electrical component that provides a specific resistance**
- **Used to control the current**

## Example

- **A 9.0 V battery is connected to a flashlight with a resistance of 200.0 ohms. What is the current running through the flashlight?**

## Resistance

- **More collisions will mean more resistance**


-  $R \propto L$

Less resistance      Greater resistance

-  $R \propto 1/A$

-  $R$  depends  
on material

-  $R \propto T$

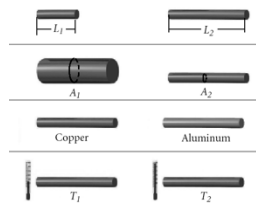

## Resistivity

- **Describes how much resistance a substance provides**

- ohm•meter

- Conductors have low resistivity


- Insulators have high resistivity

- P. 591

## Resistivity

- **Temperature also affects the resistivity of a substance**
  - Metals-Resistivity increases with T
  - Semiconductors-decreases with T
- **Temperature coefficient of resistivity -  $\alpha$**

## Superconductors

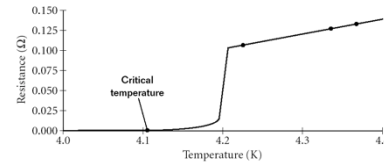

- **Materials that have a resistance of zero at or below a critical temperature**

## Drift Velocity

- **Electric Field sets charges in motion**
- **Electric field is established at almost the speed of light**
- **Charges travel more slowly**

## Drift Velocity

- **Electrons do not travel in a straight line**
  - Repeated collisions with vibrating atoms cause zigzagging
- **Despite collisions electrons still move at a net velocity**
  - **Drift velocity**
    - *very slow*

## Questions

- **What is Work?**
- **What is Work measured in?**
- **What is Power?**
- **What is Power measured in?**

## Energy Transfer

- **Circuit with a battery and light**
  - **Battery provides electrical potential energy**
  - **Light changes it to light and heat**

## Electric Power

- Rate of conversion of electrical energy

## Example Problem

- A 100.0 W light bulb is connected to 120 V potential difference.
  - What is the resistance of the light bulb?
  - What is the current flowing through the light bulb?

## Example Problem

## Kilo-watt hours

- Power companies charge for energy, not power
- Energy delivered in 1 hour at a constant rate of 1 kW

$$1kW \cdot h = 3.6 \times 10^6 J$$


## Example

- How much does it cost to operate a 60 W light bulb for 1 week if the cost of electricity is \$0.08/kW·h?

## Example
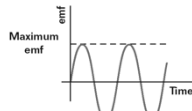
## Alternating Current-V

- Potential difference would oscillate between + and - peak or maximum values



- 60 Hertz or 60 cycles per second
  - US, Canada, & Central America
- 50 Hertz or 50 cycles per second
  - Most of the rest of the world

## Alternating Current-I


- Current would also oscillate between + and - peak or maximum values

## Alternating Current-P

- Power would also oscillate between zero and a positive maximum
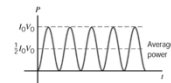
## Alternating Current-P

- Since power fluctuates, it is customary to consider the average power



Cutnell & Johnson  
Wiley Publishing  
Physics 5th Ed.  
Figure 20.12 (W157)  
© M. J.

## Root Mean Square Current

- Average magnitude of Alternating current
- Amount of direct current that dissipates as much energy as alternating current during a complete cycle

## Root Mean Square Potential Difference

- Average magnitude of alternating potential difference
- Amount of direct potential difference that dissipates as much energy as alternating potential difference during a complete cycle

## **Alternating Current**

- **Calculations for AC use the same formulas as for DC, but**
  - **Resistance doesn't change**
  - **Replace I and V with  $I_{rms}$  and  $V_{rms}$**

## **Series Wiring**

- **Circuit that contains only one possible path**
- **No components will function if one element is broken**

## **Series - Current**

- **Current will be the same in each Resistor**

## **Series - Voltage**

- **Total potential difference will be the sum of the potential difference of all resistors**

## **Series - Resistance**

## **Series - Resistance**

- **Equivalent resistance increases as more components are added**

### **Parallel**

- **Circuit that contains more than one possible path**
- **One path can be broken and the others still operate**

### **Parallel - Voltage**

- **Each path operates independently**
- **Each path uses the entire potential difference**

### **Parallel - Current**

- **Each path will carry a portion of the current**

### **Parallel - Resistance**

### **Parallel - Resistance**

- **Equivalent resistance decreases as more components are added**

### **Power in Parallel & Series**

- **All components use some energy**
- **Total energy converted will include all components**

## **Complex Resistor Combinations**

- **Most Circuits contain combination of series & parallel**

## **20-3 Complex Resistor Combinations**

### **How to solve**

#### **1. Find equivalent resistance for entire circuit**

1. **Combine Parallel resistors**
2. **Combine series resistors**
3. **Repeat until single resistance**

#### **2. Find all totals (I, $\Delta V$ , P)**

#### **3. Work backward to find each individual value**